

Contents

Preface

viii

1. The Triode Gain Stage	1
1.1: Basic Operation of Triodes	2
1.1.1: Anode Characteristics and Grid Curves	3
1.1.2: The Safe Operating Area	5
1.2: The Valve Constants	7
1.2.1: Internal Anode Resistance, r_a	7
1.2.2: Amplification Factor, μ	8
1.2.3: Transconductance, g_m	9
1.3: Amplification	10
1.3.1: The DC Load Line	10
1.3.2: Biasing	12
1.3.3: The Cathode Load Line	14
1.3.4: The Cathode Bypass Capacitor	15
1.3.5: The AC Load Line	17
1.3.6: Oscillation and Grid Stoppers	19
1.3.7: Component Types and Ratings	20
1.4: Clipping	22
1.4.1: Cut-Off Clipping	22
1.4.2: Grid-Current Clipping	23
1.5: Design Equations:	24
1.5.1: Equivalent Circuits	25
1.5.2: Fully Bypassed Gain	25
1.5.3: Degenerated (Unbypassed) Gain	27
1.5.4: Impedance Matching and Bridging	28
1.5.5: Fully Bypassed Output Impedance	29
1.5.6: Degenerated (Unbypassed) Output Impedance	29
1.5.7: Input Impedance and the Miller Effect	30
1.5.8: Power Supply Rejection Ratio (PSRR)	31
1.6: Valves in Parallel	33
1.6.1: Characteristics of Parallel Valves	33
1.6.2: The Common-Anode Mixer	33
1.7: Local Shunt Feedback	35
1.7.1: The Anode Follower	37
1.7.2: The Virtual-Earth Mixer	38
1.7.3: Negative Feedback and Distortion	38
 2. More Preamp Essentials	 40
2.1: Guitar Pickups	47
2.1.1: Pickup Frequency Response	42
2.1.2: Active Guitar Pickups	43
2.1.3: Piezoelectric Pickups	43
2.2: The Input Stage	44

2.2.1: Fender	45
2.2.2: Marshall	46
2.2.3: Dual Input Channels	47
2.3: More on Clipping and Distortion	47
2.3.1: Harmonic Distortion	47
2.3.2: Harmonic Distortion in Triodes	49
2.3.3: Intermodulation Distortion	50
2.4: Bias Shift and Blocking Distortion	52
2.4.1: Bias Shift	52
2.4.2: Blocking Distortion	54
2.4.3: Minimising Blocking Distortion	56
2.5: Interstage Networks	57
2.5.1: Interstage Filters	58
2.5.2: Bright Capacitors	60
2.5.3: Anode Bypass Capacitors	61
2.5.4: Passive Mixing	62
2.5.5: Passive Diode Clipping	63
2.6: An Approach to Preamp Design	64
2.6.1: A High-Gain Design	66
2.7: Master Volume Controls	68
2.7.1: Simple Master Volume	68
2.7.2: Post Phase-Inverter Master Volume	69

3. Tone Controls 72

3.1: General Considerations	72
3.1.1: Position in Circuit	72
3.1.2: Impedance Considerations	73
3.1.3: Impedance Scaling	74
3.1.4: Frequency Range	75
3.1.5: Tone Stack Defeat / Lift	77
3.2: Simple Treble Controls	77
3.3: Simple Bass Controls	80
3.4: Simple Middle Control	80
3.5: Tilt Control	83
3.6: Bandmaster Tone Stack	85
3.7: James Tone Stack	85
3.8: Passive Baxandall Tone Stack	87
3.9: Active Baxandall Tone Controls	88
3.10: FMV Tone Stack	89

4. The Cathode Follower 92

4.1: Design Equations	92
4.1.1: Gain	92
4.1.2: Input Impedance	93
4.1.3: Output Impedance	94
4.1.4: PSRR	95
4.2: Oscillation and Stoppers	95

4.3: Design for AC Coupling	96
4.3.1: Cathode Bias	97
4.3.2: Fixed Bias	98
4.4: Design for DC Coupling	100
4.4.1: Cathode Followers in Guitar Amps	102
4.4.2: Grid-Cathode Arc Protection	104
4.5: Bootstrapping for More Gain	105
4.6: MOSFET Followers	107
4.7: Safe Line Outputs	108
4.7.1: Effects Loop	109
5. The Pentode Gain Stage	111
5.1: A Brief History of Pentodes and Tetrodes	111
5.2: The Screen Grid	113
5.2.1: The Effect of Screen Voltage	113
5.2.2: The Effect of Screen Current	114
5.2.3: The m-Ratio	115
5.2.4: Deriving Grid Curves for any Screen Voltage	116
5.3: The Vox <i>AC15</i> Input Stage	118
5.4: The Effect of Load on Tone	120
5.5: Design Equations	121
5.6: Pentodes Connected as Triodes	123
5.6.1: Pentode-Triode Morph Control	123
6. The Cathodyne Phase Inverter	125
6.1: Basic Operation of the Cathodyne	126
6.2: Design Equations	126
6.2.1: Gain	126
6.2.2: Input Impedance	127
6.2.3: Output Impedance	128
6.2.4: PSRR	129
6.3: Designing a Cathodyne	130
6.3.1: Biasing	131
6.4: Avoiding Unpleasant Distortion Effects	133
7. The Long-Tailed-Pair	135
7.1: Basic Operation of the Long-Tailed Pair	136
7.2: Design Equations	137
7.2.1: Gain	137
7.2.2: Input Impedance	137
7.2.3: Output Impedance	138
7.2.4: PSRR	139
7.2.5: CMRR	139
7.3: Designing a Long-Tailed Pair	140
7.3.1: Dissimilar Anode Resistors	142
7.4: Bias and Overdrive	143
7.4.1: Scale Control	146

7.5: Adding Global Negative Feedback	147
7.5.1: Dealing with Instability	149
7.5.2: Presence Control	151
8. Tremolo	153
8.1: The Phase-Shift Oscillator	154
8.1.1: On/Off Switching	156
8.1.2: MOSFET Oscillator	158
8.2: Modulation	159
8.2.1: Optocoupler / LDR	159
8.2.2: Single-Ended Bias Modulation	161
8.2.3: Push-Pull Bias Modulation	163
8.2.4: Phase-Inverter Modulation	165
8.2.5: Suppressor-Grid Modulation	165
8.3: Fixing Thumping and Ticking	166
8.3.1: Ticking in Vintage Fenders	167
9. Spring Reverb	169
9.1: Constant-Voltage vs. Constant-Current Drive	171
9.2: Classic Fender Reverb Driver	172
9.2.1: Improving PSRR	174
9.3: Push-Pull Reverb Driver	174
9.4: Transformerless Reverb Drivers	176
9.5: Dwell	177
9.6: Recovery and Mixing	178
9.6.1: One-Bottle Reverb	181
10. Single-Ended Output Stages	182
10.1: Output Transformers	182
10.1.1: Voltage and Impedance Ratio	183
10.1.2: Measuring an Unknown Transformer	183
10.1.3: Load Impedance Mismatching	185
10.1.4: Bandwidth and Strays	186
10.2: Output Transformer Protection	188
10.2.1: Fusing	188
10.2.2: Flyback Protection	189
10.2.3: Catching Diodes	190
10.2.4: MOVs	190
10.3: Loudspeakers and Loads	191
10.3.1: Dummy Loads	192
10.4: Single-Ended Triodes	194
10.4.1: Load Lines for Single-Ended Power Stages	194
10.4.2: The Optimum Load for Triodes	196
10.4.3: Output Impedance	198
10.4.4: PSRR	199
10.5: Single-Ended Pentodes / Tetrodes	199
10.5.1: The Optimum Load for Pentodes / Tetrodes	200

10.5.2: Design by Datasheet	201
10.5.3: Fixed vs. Cathode Bias	204
10.5.4: The Cathode Bypass Capacitor	206
10.5.5: Reactive Loads	207
10.5.6: Protecting the Screen Grid	209
10.6: Design for Guitar Amps	211
10.6.1: Design Process	212
10.6.2: The Fender <i>Champ</i>	214
11. Push-Pull Output Stages	216
11.1: Amplifier Class	217
11.1.1: Class-A	217
11.1.2: Class-AB	218
11.1.3: Class-B	218
11.1.4: Class-C	219
11.2: Push-Pull Pentodes / Tetrodes	219
11.2.1: Design by Datasheet and the Vox <i>AC15</i>	219
11.2.2: Push-Pull Load Lines	221
11.2.3: Calculating Output Power	224
11.2.4: Measured Power and Sag	224
11.2.5: Reactive Loads	225
11.3: Biasing	226
11.3.1: Cathode vs. Fixed Bias	226
11.3.2: Shared vs. Separate Cathode Bias	227
11.3.3: Bias Imbalance	228
11.3.4: Measuring and Setting Bias Current	228
11.3.5: Hybrid or Mixed Bias	230
11.3.6: Cross-Coupled (Garter) Bias	231
11.3.7: Bias Shift and Crossover Distortion	233
11.4: Ultra-Linear	235
11.5: A 50W Design Example	236
11.5.1: Design Process	237
11.5.2: Measured Performance	240
11.5.3: Adding Global Feedback	241
12. The Power Supply	244
12.1: Essentials of Rectification	245
12.1.1: Average DC Output Voltage	246
12.1.2: Ripple Voltage and Reservoir Capacitance	248
12.1.3: Ripple Current	249
12.1.4: Power Factor	250
12.1.5: Diode Ratings	252
12.1.6: Cheat-Sheet Summary	253
12.2: Valve Rectifiers	254
12.2.1: Heater Supply	254
12.2.2: Electrical Ratings	255
12.2.3: Limiting Resistance	257

12.2.4: Voltage Drop and Sag	258
12.2.5: Care and Protection of Valve Rectifiers	259
12.2.6: Hybrid Bridge Rectifier	260
12.3: Voltage Doubling	260
12.3.1: Bipolar / Dual Two-Phase Rectifier	261
12.4: Switching and Fusing	262
12.4.1: Standby-Switch Origins	263
12.4.2: Standby and Valve Lifetime	264
12.4.3: Least-Worst Standby Switches	265
12.4.4: Fusing	267
12.5: Smoothing Filters	268
12.5.1: Design Choices	269
12.5.2: LC vs. RC Filtering	272
12.6: Heater Supplies	273
12.6.1: Electrical Heater Balancing	274
12.6.2: Heater Elevation	275
12.6.3: Dropping Heater Voltage	276
12.6.4: DC Heater Supply	276
12.6.5: Series Heaters	277
12.7: Bias Supplies	278
12.7.1: Traditional Bias Supplies	278
12.7.2: How Much Bias Voltage?	280
12.7.3: Full-Wave Bias Supply	280
12.7.4: Capacitor-Coupled (Non Centre-Tapped) Bias Supplies	281
12.7.5: Bias Balance	282
12.8: Changing the Wall Voltage	283
13. Signal Switching	285
13.1: Series and Shunt Switching	285
13.2: Clicks, Pops and Thumps	287
13.3: Relays	288
13.3.1: Audio Switching with Relays	289
13.3.2: Control Circuits for Relays	290
13.4: Solid-State Relays	292
13.4.1: Audio Switching with SSRs	293
13.4.2: Control Circuits for SSRs	293
13.5: JFET Gain-Boost Switch	295
13.6: Low-Voltage DC Power	297
14. Layout and Grounding	298
14.1: General Layout	298
14.1.1: Hum and the Headphone Test	300
14.1.2: Wiring and Lead Dress	301
14.2: Grounding	303
14.2.1: Earthing and Safety	304
14.2.2: Ground Loops	306
14.2.3: The Rectifier	306

14.2.4: Signal Currents	308
14.2.5: Bus Grounding	309
14.2.6: Star Grounding	310
14.2.7: Miscellaneous Ground Connections	311
15: Appendix	314
15.1: Some Valve Pinouts	314
15.2: Some Triode Grid Curves	315
15.3: Some Screen-Grid Curves	317
Index	319